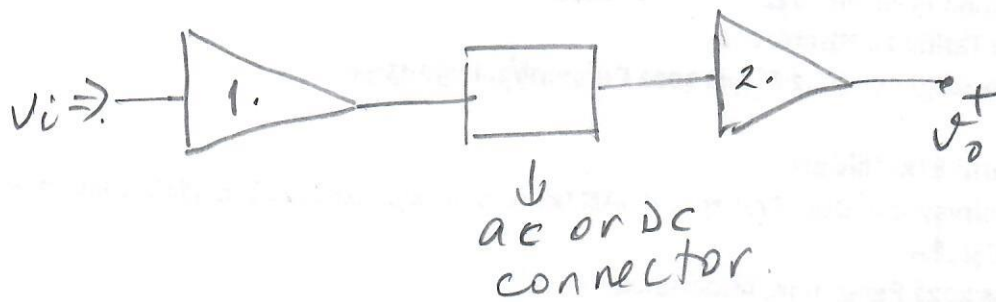



multistage Amplifiers

(1)


- AC amplifiers
- DC amplifiers.



1/ AC Amplifiers.

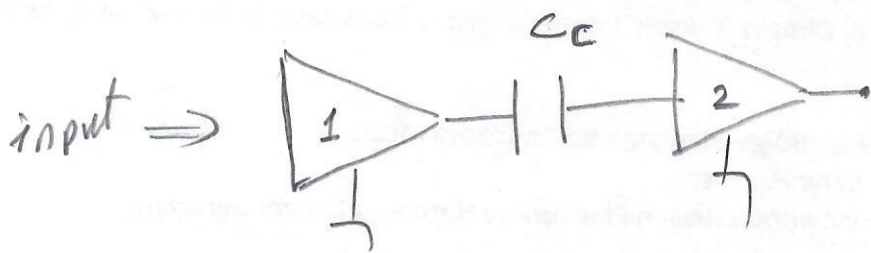


capacitor or a transformer. used.

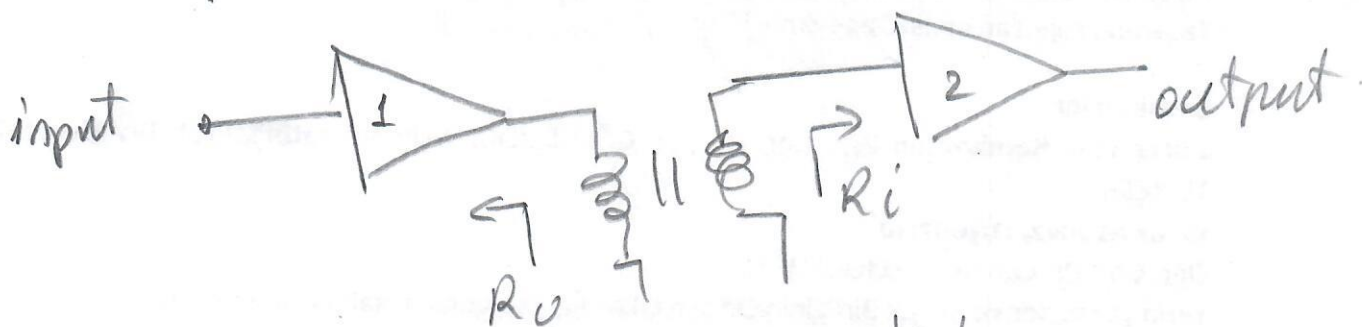

$R_o = R_i$ is expected.

Frequency - Gain graphic

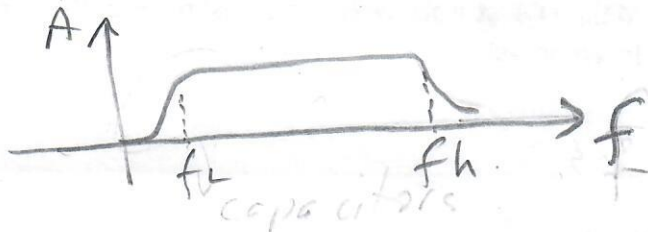


At low frequencies "C" are effective
 "L" high frequencies $L \Rightarrow Z = \omega L$

$\omega \rightarrow 0 \Rightarrow X_L \Rightarrow 0$
 $\omega \rightarrow \infty \Rightarrow X_L = \infty$

So, at low frequencies $X_C = \frac{1}{\omega C} \Rightarrow A \downarrow$
 " " high " " $X_L = \omega L \Rightarrow A \downarrow$

For the circuit shown;

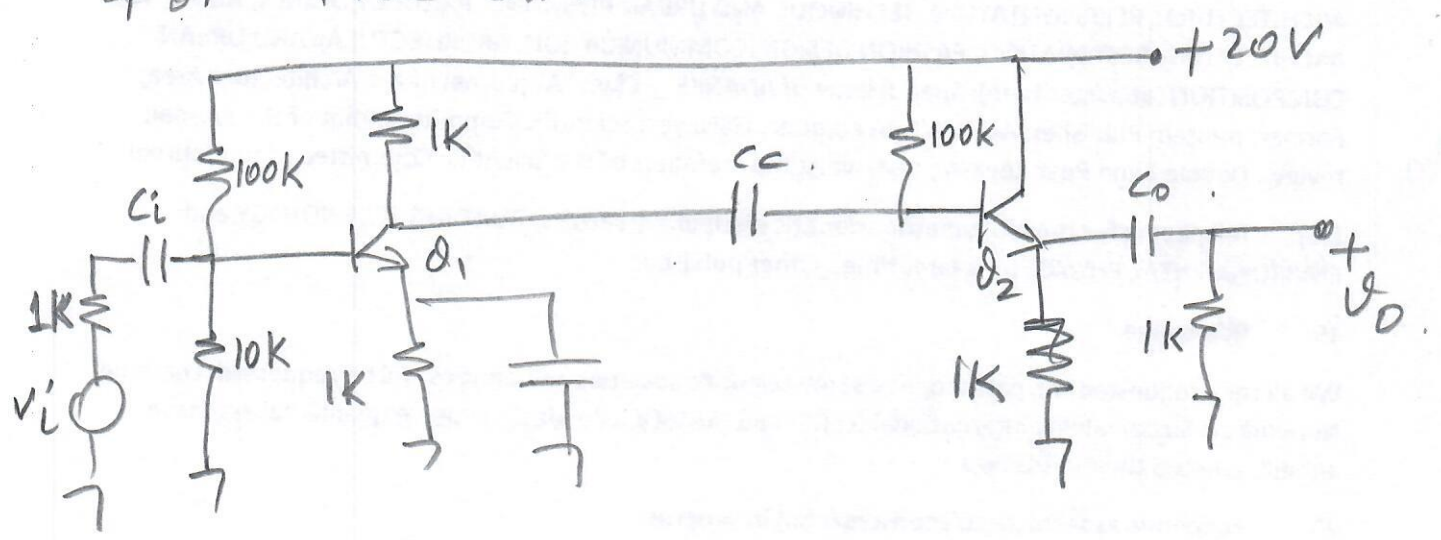

$h_{fe} = 100, V_o = 0.6V, I_{co} = 0A, V_{CE SAT} \approx 0V$
 (capacitors are short for a.c)


a) Draw AC and DC load lines

b) $A_v = \frac{v_o}{v_i}$


c) $V_{imax} = ?$

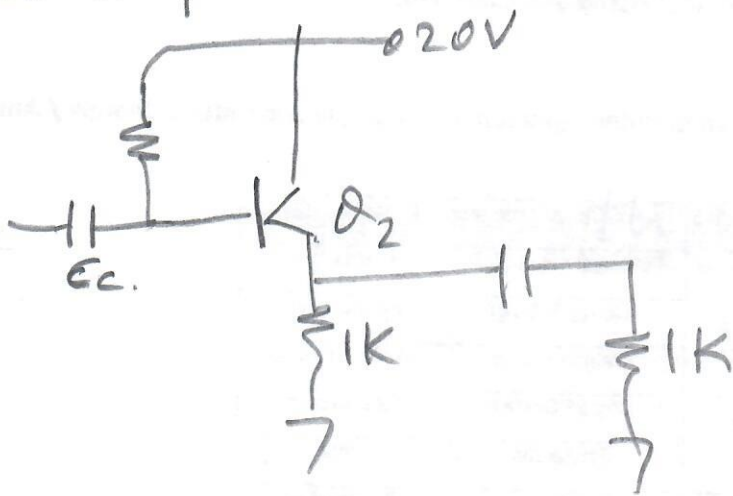(3)

Let us start the solution from the output



DC Analysis / DC equivalent circuit:

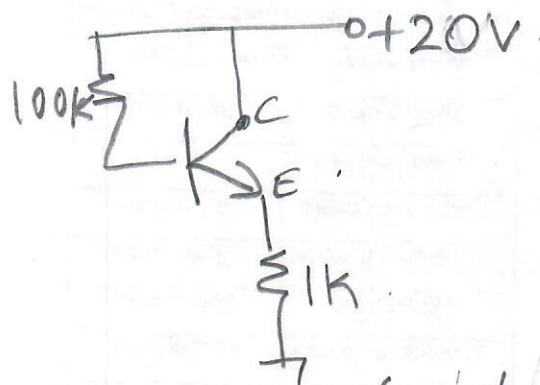

KVL: for the input loop:

$$20 = 100k \cdot I_{BQ} + V_0 + 1k(1 + 100) I_{BQ}$$


$$I_{BQ} = 97 \mu A \Rightarrow I_{CQ} = h_{fe} \cdot I_{BQ} = 9,7 \text{ mA}$$

$$V_{CEQ} = 20 - 1k \cdot I_{CQ} \Rightarrow \text{KVL (output)}$$

$$V_{CEQ} = 10,3 \text{ V} \approx 10 \text{ V}$$

ac analysis

(4)

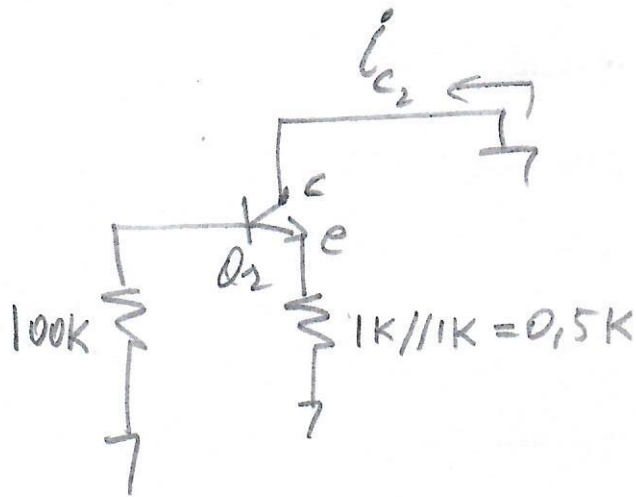

$$V_{CE2} = -500 i_{c2}$$


$$i_{c2} = I_{CQ2} + i_{c2}$$

$$V_{CE2} = V_{CEQ2} + v_{ce2}$$

$$V_{CE2} = V_{CEQ2} - 500 \Omega (i_{c2} - 9,7 \text{ mA})$$

$$V_{CE2} = 10 + 500 \times 9,7 \cdot 10^{-3} - 0,5 \text{ K} \cdot i_{c2}$$
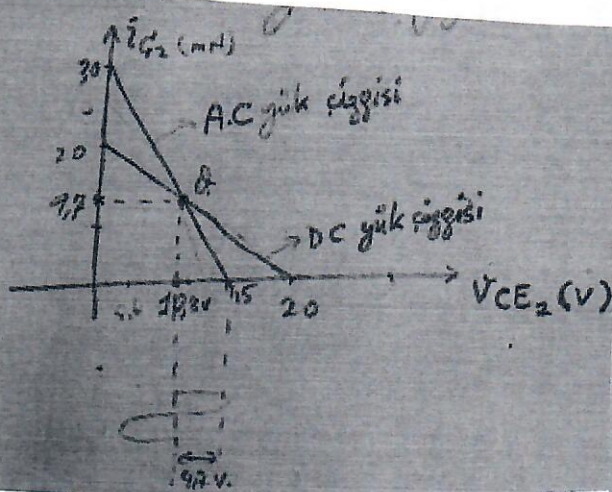
$$\boxed{V_{CE2} = 15 - 0,5 \text{ K} \cdot i_{c2}} \quad \text{ac+dc eq.}$$




$$v_{ce} = -v_{ce2}$$

$$v_{ce} = 4,7 \sin \omega t$$


efen antresenisi
(yağya $V_{CE2} = 15 - 0,5 \text{ K} i_{c2}$)

$$i_{c2} = 0 \quad V_{CE2} = 15$$

$$V_{CE2} = 0 \quad i_{c2} = 20$$

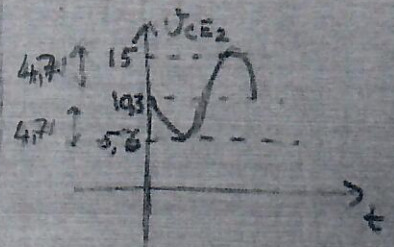


Let us now solve the 1. amplifier. (5)

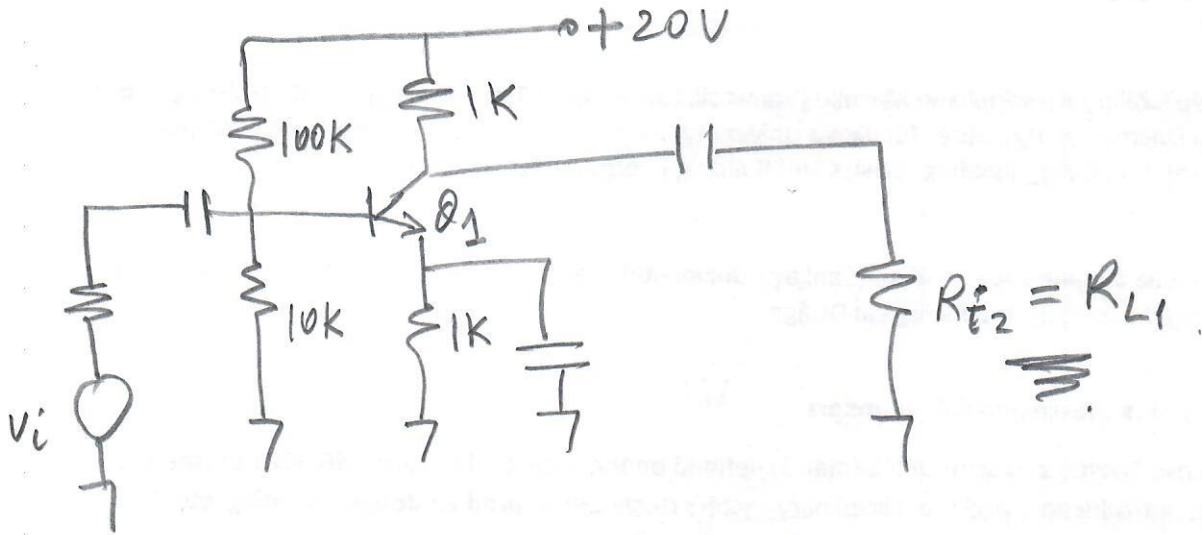


Note that $R_{i2} = R_{L1}$

According to the common emitter of Q_2

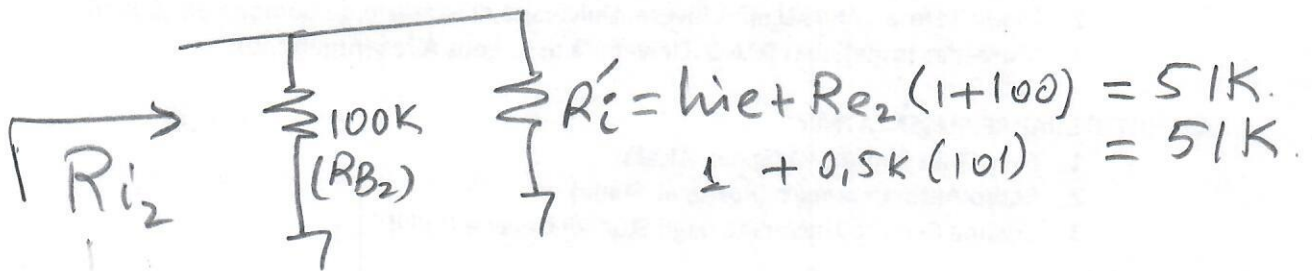


$$R_{i2} = 100k // R'_i = 100k // 51k \approx 33k$$

DC Analysis of first amplifier; 20V

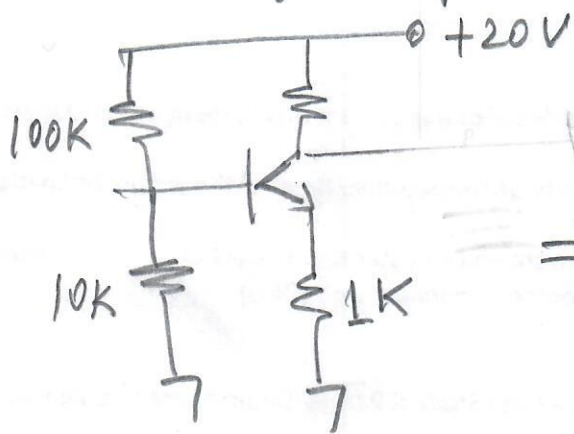

\Rightarrow

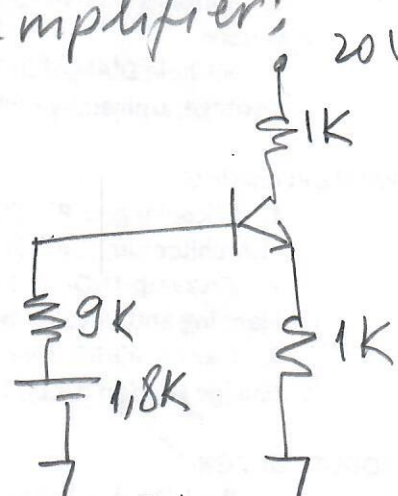


$$I_{BQ1} = \frac{1.8 - 0.6}{9k + (101)k} = 13 \mu A$$

$$I_{CQ1} = h_{FE} I_{BQ1} = 1.3 mA$$

$$V_{CEQ1} = 20 - 2k I_{CQ1} = 17.4 V$$

ac. analysis:

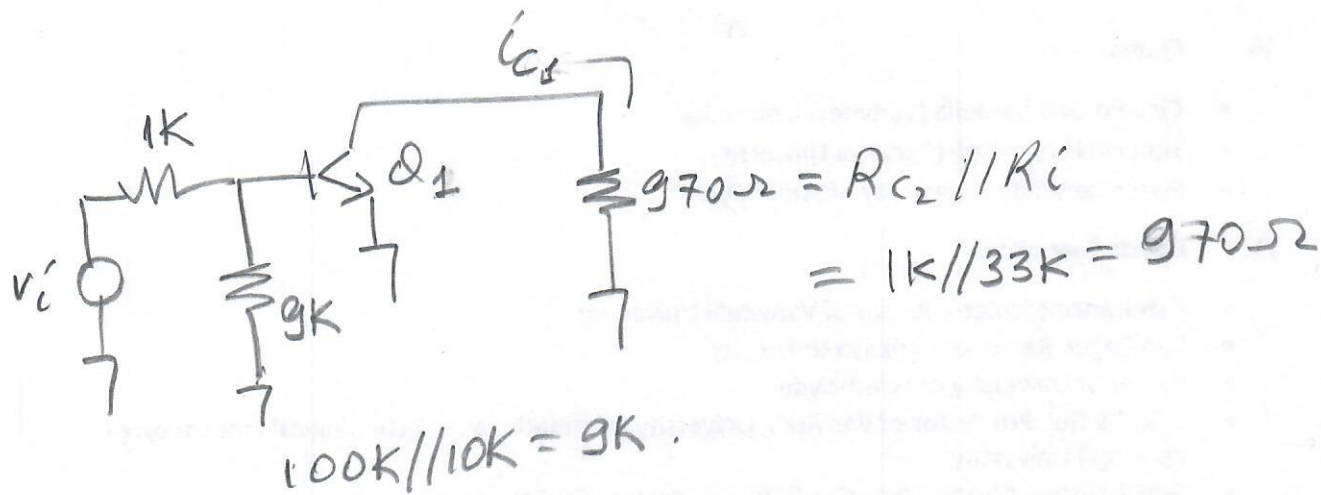


ac equation



$$v_{ce1} = -970 i_{c1}$$

$$v_{ce1} - v_{ceQ1} = -970 (i_{c1} - I_{cQ1})$$

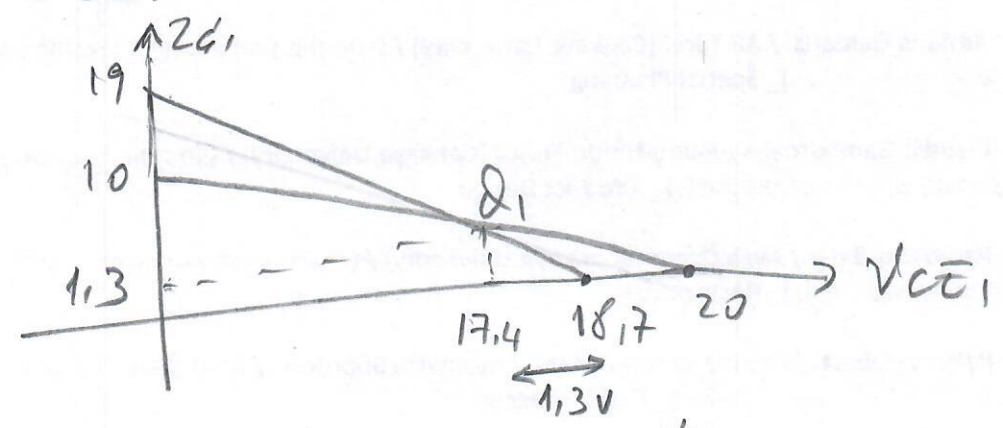
$$v_{ce1} = 17,4 + 970 I_{cQ1} - 970 i_{c1}$$




$$v_o = 1,3 \sin \omega t$$

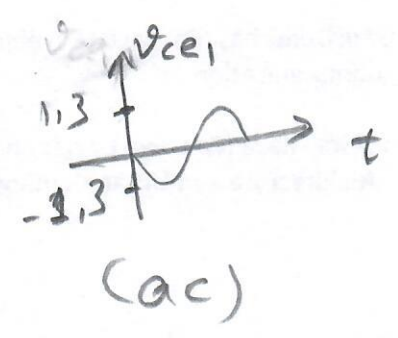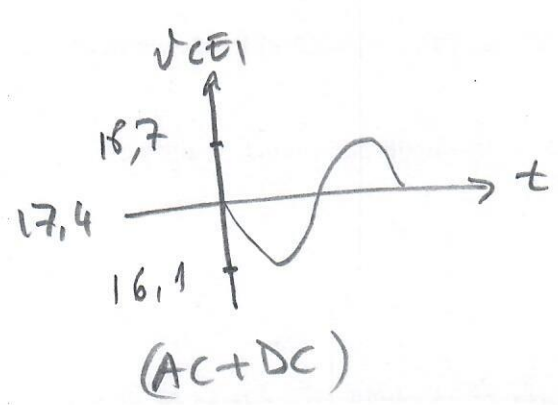

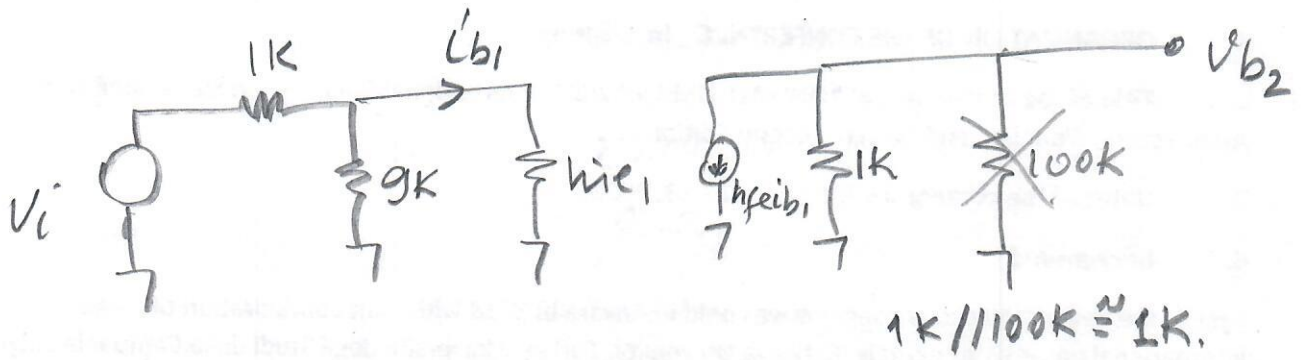To calculate the gain of the 1. amplifier, the equivalent circuit:


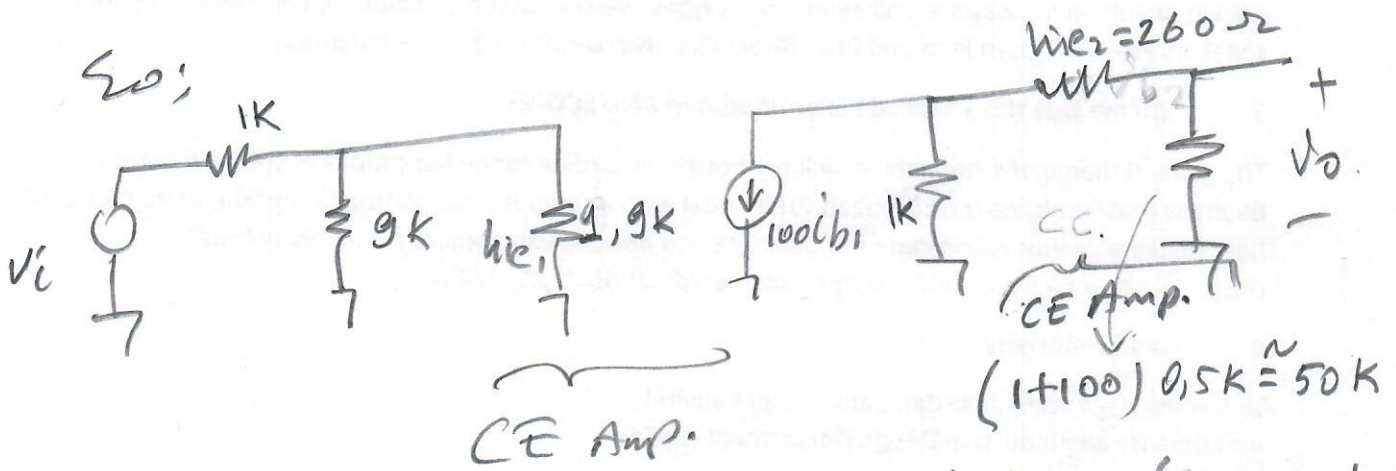
$$h_{ie2} = 260 = \frac{h_{fe} \cdot 26 \text{ mV}}{I_{E2}}, \quad h_{ie1} = 1,9 \text{ K (calculated)}$$



$$V_o \approx V_{b2} \quad (h_{ie2} \text{ neglected})$$

Overall voltage gain of the Amplifier:

$$A_v = A_{v1} \times A_{v2}$$

$$V_{b2} = -1 \text{ K} (h_{fe} \cdot i_{b1}) \quad \text{(almost total current passes through 1K, because other resistance (50K+260Ω))}$$

$$\frac{V_{b2}}{i_{b1}} = -100 \cdot 10^3$$

$$\frac{i_{b1}}{V_i} = 0,321 \cdot 10^{-3} \quad \text{Thus:}$$

$$A_{v1} = \frac{V_{b2}}{V_i} = \frac{V_{b2}}{i_{b1}} \cdot \frac{i_{b1}}{V_i} = -100 \cdot 10^3 \times 0,321 \cdot 10^{-3} \approx -32$$


$$A_{v2} = 1 \quad \Rightarrow \quad A_v = A_{v1} \cdot A_{v2} = -32$$

8


To find $V_{i\max} = ?$

That is the maximum voltage applied so that output is not distorted.

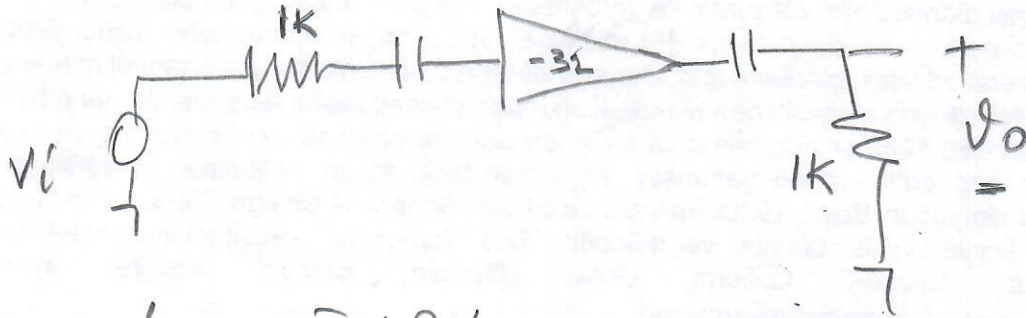In other words, beyond $V_{i\max}$, output voltage starts distorting.



$$V_{CE1} = \pm 1.3V$$

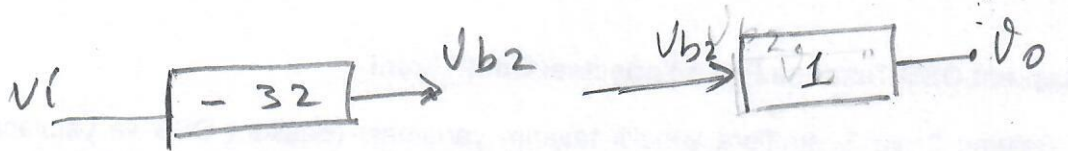


$$V_o = V_{b2} = V_{CE2}$$

$$A_v = \frac{V_o}{V_i} = -32 \Rightarrow V_i = \frac{1.3}{32} = 40.5 \text{ mV}$$

$$V_{i\max} = \pm 40.5 \text{ mV}$$

DC Amplifiers.

9

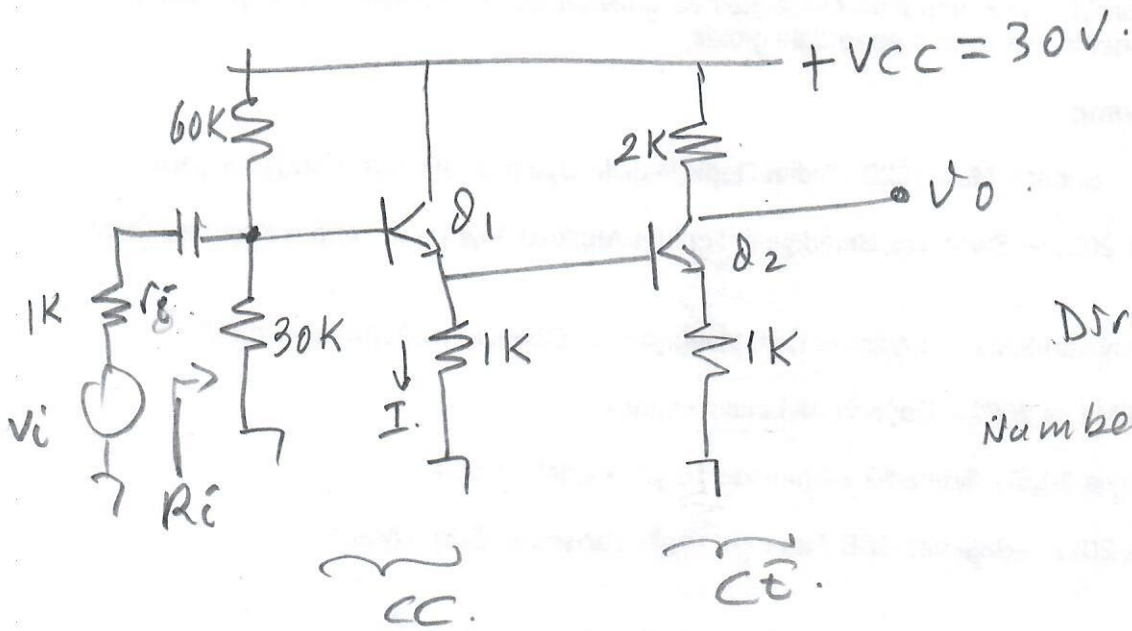

Direct connection
Number of stages ≤ 3

Solution:

CC $\Rightarrow A_v = 1$


CE Approximate solution
 $A_{v2} \approx -\frac{R_c}{R_e} = \frac{2K}{1K} = -2$

$R_i \gg r_i \Rightarrow$

$V_{b1} = V_i$

Question: Find $V_o (P-P) = ?$
 $h_{fe1} = h_{fe2} = 20, V_o = 0.6V, I_{co} = 0, V_{CE_{SAT}} = 0.$

DC equivalent circuit/DC Analysis

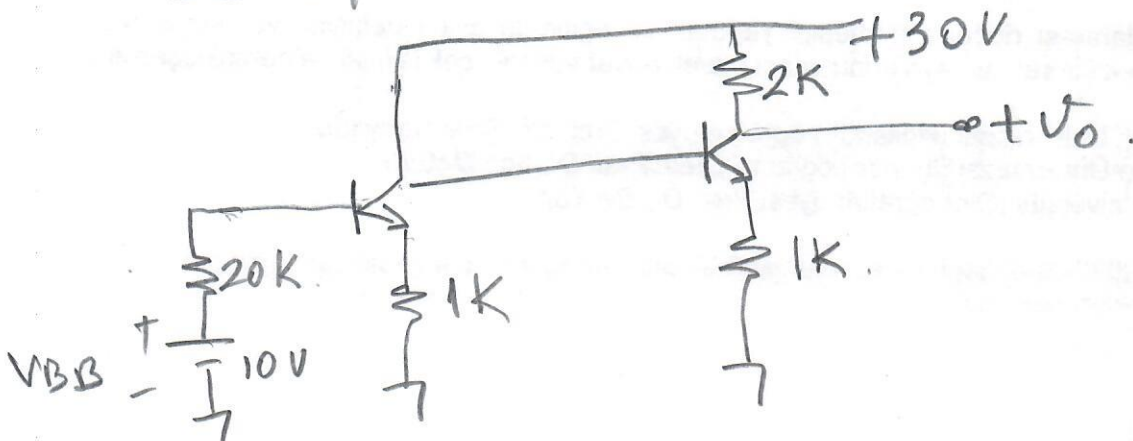

$20K = 30K // 60K \Rightarrow R_{TH}$
 $V_{TH} = V_{BB} = \frac{30 \cdot 30}{90} = \frac{900}{90} = 10V$

$$I \gg I_{BQ2} \Rightarrow I_{E1} = I$$

$$I_{EQ1} = \frac{10 - 0,6}{\frac{20K}{21} + 1K} = 4,81 \text{ mA}$$

(1+hfe)

$$V_{EQ1} = 1K \cdot I_{EQ1} = 4,81 \text{ V}, \quad V_{EQ2} = V_{EQ1} - 0,6 \text{ V}$$
$$V_{EQ2} = 4,21 \text{ V}$$

$$I_{EQ2} = \frac{V_{EQ2}}{1K} = 4,21 \text{ mA}$$

$$I_{BQ2} = \frac{I_{BQ2}}{1+hfe} = \frac{4,21}{21} = 0,2 \text{ mA}$$

$$I_{EQ1} \approx I = 4,81 \text{ mA} \gg I_{BQ2} = 0,2 \text{ mA} \dots \dots 0,1K \cdot V$$


$$V_{CE2} = 30 - 3K I_{CQ2} = 30 - 3K(4,21 \text{ mA}) = 17,37 \text{ V}$$

$$V_{CQ2} = 30 - 2K(4,21 \text{ mA}) = 21,58 \text{ V}$$


$$V_{CE1} = 30 - 1K \times \underbrace{4,81 \text{ mA}}_I = 25,19 \text{ V}$$

so, we can plot load lines:


$$V_{CE2} = 30 - 3K I_{CQ2}$$

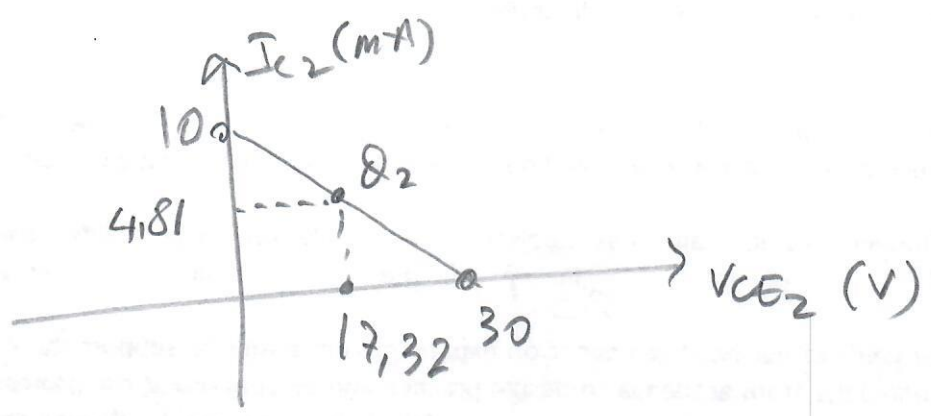

$$V_{C2Q} = V_o = 30 - 2K I_{C2}$$

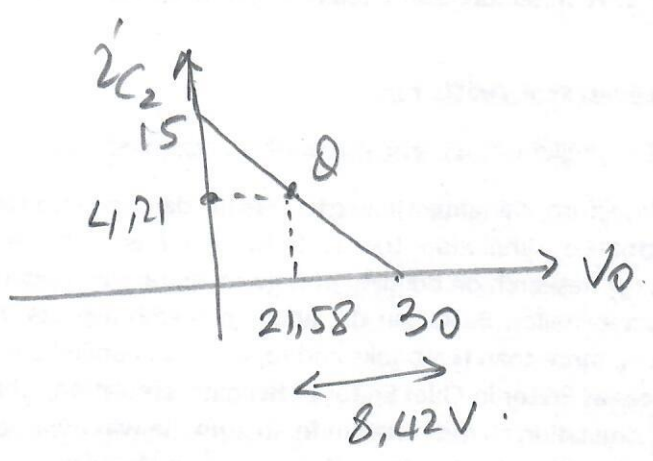

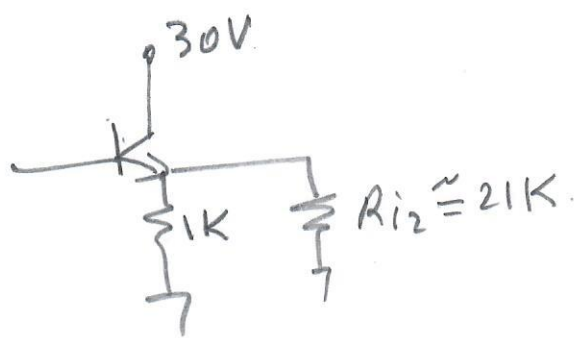
$$R_{i2} = h_{ie2} + (1 + h_{fe}) R_e = 118 + 21K \approx 21K$$



$$\begin{aligned} \text{So, } V_{CE1} &= V_{CC} - 1K \cdot I_{C1} \\ &= 30 - 1K \cdot I_{C1} \end{aligned}$$

$$V_{ce1} = 1K \cdot i_{c1}$$

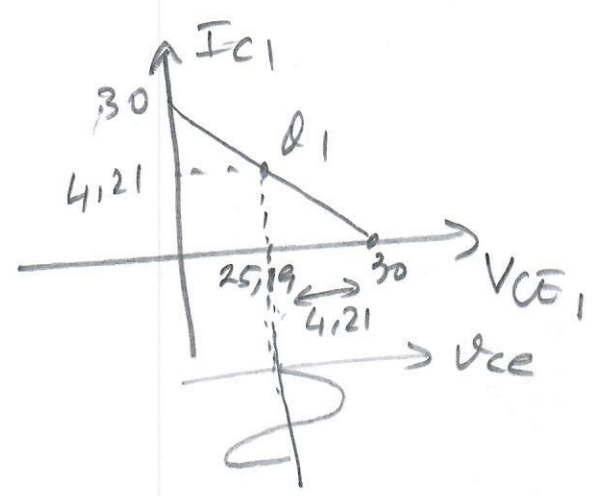

$$V_{ce2} = -(R_c + R_e) i_{c2}$$

$$i_{c2} (P-P) = 2 \times 4,21 \text{ mA} = 8,42 \text{ mA}$$

$$V_o (P-P) = 8,42 \times \underset{\downarrow R_c}{2 \text{ K}} = 16,84 \text{ Volt}$$

To find $V_i = ?$

$$A_v = A_{v1} A_{v2} = 1 \cdot (-2) = -2$$


$$\frac{V_o}{V_i} = A_v = -2 = \frac{16,84 (P-P)}{V_i}$$

$$V_i = 8,42 (P-P)$$

Cascode Amplifiers.

At high frequencies CB connection has better frequency response; i.e. larger band width.

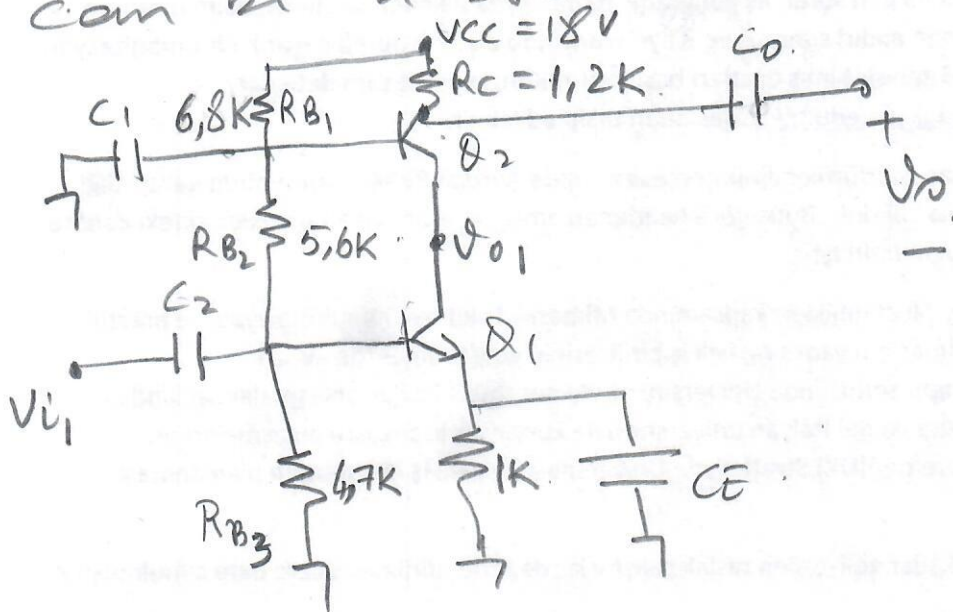
CB has comparatively lower input impedance, so a cascode amplifier can be a solution.



$\beta_1 = \beta_2 = 100$

$I_{E2} = I_{E1}$ or $I_{C2} = I_{C1} \Rightarrow I_{B2} = I_{B1}$

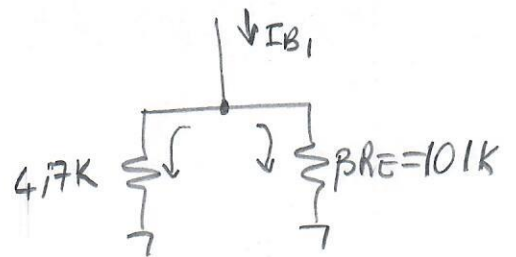$V_{B1} = \frac{R_{B3} \cdot V_{CC}}{R_{B1} + R_{B2} + R_{B3}} = \frac{84.6}{17.1} = 4.95V.$



$I_{E1} \approx \frac{V_{E1}}{R_E} = \frac{V_{B1} - V_{BE}}{R_E} = \frac{4.95 - 0.7}{1K} = 4.25mA$

$I_{4.7K} \approx I_{B1}$

$h_{ie1} = \frac{25mV \cdot h_{fe}}{I_{E1}} = 612 \Omega$

Since $I_{E1} = I_{E2} \Rightarrow h_{ie1} = h_{ie2}$

$h_{ib2} \approx \frac{h_{ie}}{h_{fe}}$

$A_{v1} = \frac{V_{o1}}{V_{i1}} \approx - \frac{h_{fe} \cdot R_L}{h_{ie1}}$


$$A_{v1} = \frac{v_{o1}}{v_{i1}} = - \frac{h_{fe} \cdot h_{ie2}}{h_{ie1}}$$

$$A_{v1} = \frac{h_{fe} \cdot h_{ie2}}{h_{fe} \cdot h_{ie1}} = -1$$

$$A_{v2} = + \frac{R_L \cdot h_{fe}}{h_{ie2}} = \frac{R_C \cdot h_{fe}}{h_{ie2}} = \frac{1.2K \cdot 100}{612}$$

$$A_{v2} \approx 196. \Rightarrow A_V = A_{v1} \cdot A_{v2} = (-1)(196) = -196.$$

DARLINGTON PAIR

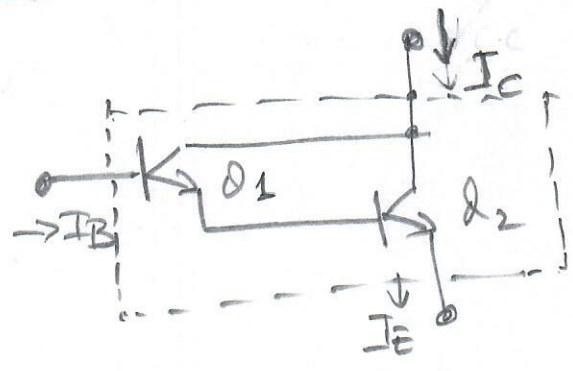

$$I_{E1} = I_{B2}$$

$$I_{C2} = h_{fe2} \cdot I_{B2} = h_{fe2} \cdot I_{E1}$$

$$I_{C1} = h_{fe1} \cdot I_{B1} = I_B$$

$$I_{E1} = (1+h_{fe}) I_{B1} = (1+h_{fe}) I_B$$

$$I_C = I_{C1} + I_{C2}$$

$$I_C = h_{fe1} I_B + h_{fe2} (1+h_{fe1}) I_B$$

$$I_C = [h_{fe1} + h_{fe2} (1+h_{fe1})] I_B$$

$$I_E = I_{E2} = (1 + h_{fe2}) I_{B2}$$

$$I_E = (1 + h_{fe2})(1 + h_{fe1}) I_B$$

if $h_{fe1}, h_{fe2} \gg 1$ so,

$$I_C = (h_{fe1} \cdot h_{fe2} + h_{fe1}) I_B$$


$$I_E \approx h_{fe1} \cdot h_{fe2} \cdot I_B \Rightarrow I_E = \beta_1 \cdot \beta_2 \cdot I_B$$

$$I_C = (1 + \beta_2) \beta_1 \cdot I_B \Rightarrow I_C = \beta_1 \cdot \beta_2 \cdot I_B$$

$$\frac{I_C}{I_B} = A_I = \beta_1 \cdot \beta_2$$


In general, $h_{fe2} < h_{fe1}$,

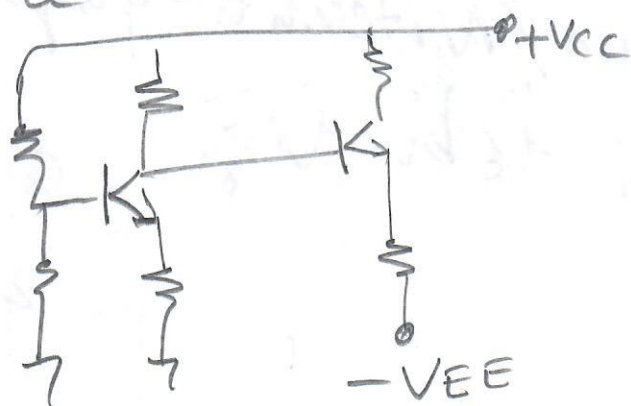Q_2 transistor goes to saturation early.
So, to prevent that, additional V_{EE} source can be used.




$$I_{EQ_{new}} = \frac{V_{E_{od_{zed}}} - V_{EE}}{R_E}$$

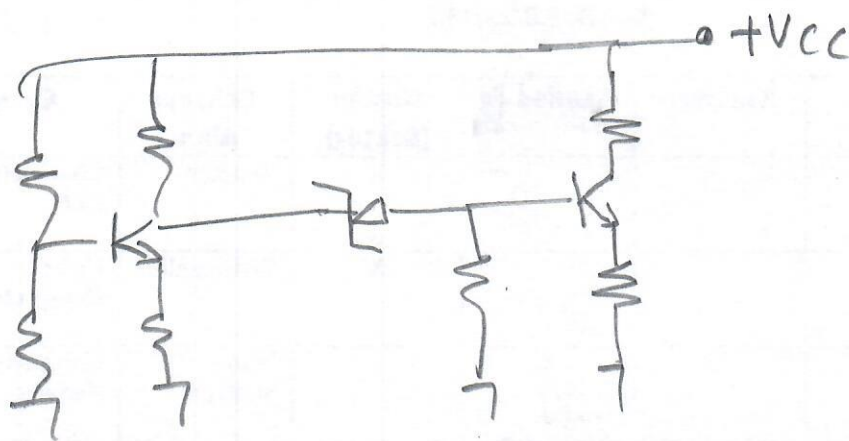other alternative is to use zener diode at the base of the Q_2 transistor, which keeps the V_{B2} constant, to set the I_{B2} .



Composite Amplifier.

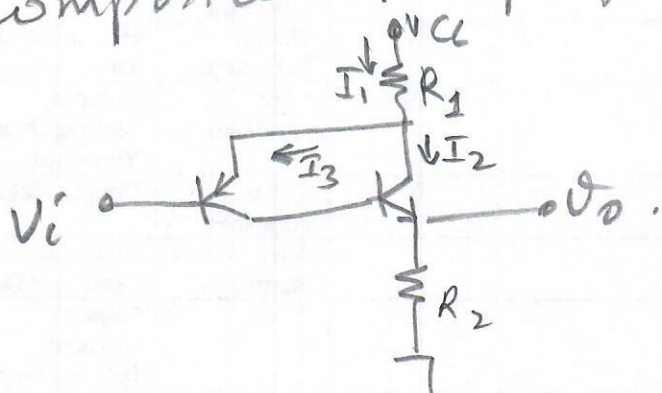

$$V_{CC} = I_1 R_1 + V_{EB} + V_i$$

$$V_{CC} = I_1 R_1 + V_o + V_i$$

$$\frac{V_{CC} - (V_i + V_o)}{R_1} = I_1 \approx \frac{V_o}{R_2} \approx I_2$$

$$V_o = \frac{R_2}{R_1} [V_{CC} - V_i - V_o]$$

→ constant
→ constant

output voltage is proportional to V_i