

Name _____
Date _____
Instructor _____

EXPERIMENT
31

Oscillator Circuits

OBJECTIVE

To measure voltage waveforms in various oscillator circuits.

EQUIPMENT REQUIRED

Instruments

Oscilloscope
DMM
Function generator
DC power supply

Components

Resistors

(3) 10-k Ω
(1) 51-k Ω
(1) 100-k Ω
(1) 220-k Ω
(1) 500-k Ω pot

Capacitors

(3) 0.001- μ F
(3) 0.01- μ F
(1) 15- μ F

ICs

- (1) 7414 Schmitt Trigger IC
- (1) 741 (or equivalent) op-amp
- (1) 555 Timer IC

EQUIPMENT ISSUED

| Item | Laboratory serial no. |
|--------------------|-----------------------|
| DC power supply | |
| Function generator | |
| Oscilloscope | |
| DMM | |

RÉSUMÉ OF THEORY

Oscillator circuits can be built using op-amps with feedback to phase-shift the output signal by 180°. Phase-shift: In a phase-shift oscillator, as shown in Fig. 31.1, three sections of resistor-capacitor are used. The resulting oscillator frequency can be calculated using

$$f = \frac{1}{2\pi\sqrt{6}RC} \text{ Hz} \tag{31.1}$$

For the op-amp to cause the circuit to oscillate requires that the op-amp gain be of magnitude 29.

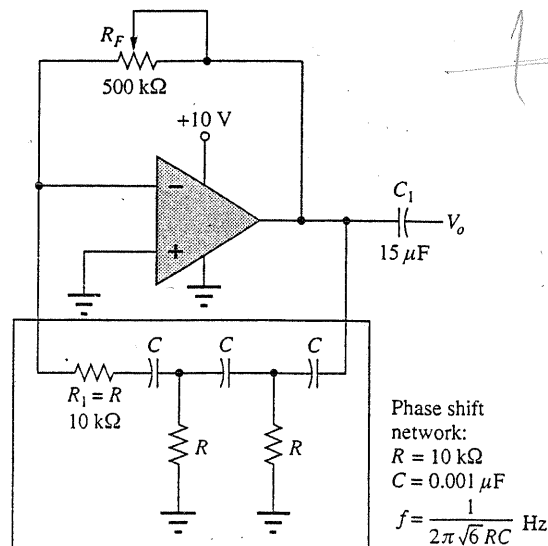


Figure 31-1

Wien-Bridge

A bridge network can be used to provide the 180° phase shift as shown in Fig. 31.2. The circuit's resulting frequency can be calculated from

$$f = \frac{1}{2\pi\sqrt{R_1C_1R_2C_2}} \tag{31.2}$$

$\frac{1}{2 \times 10^4 \times \sqrt{6} \times 10^5 \times 10^{-9}}$
 $\frac{10^4}{6.28 \times 2.45}$

$\frac{1}{2\pi\sqrt{6} \times 10^5 \times 10^{-9}}$
 $\frac{10^4}{6.28 \times 2.45}$

Handwritten signature

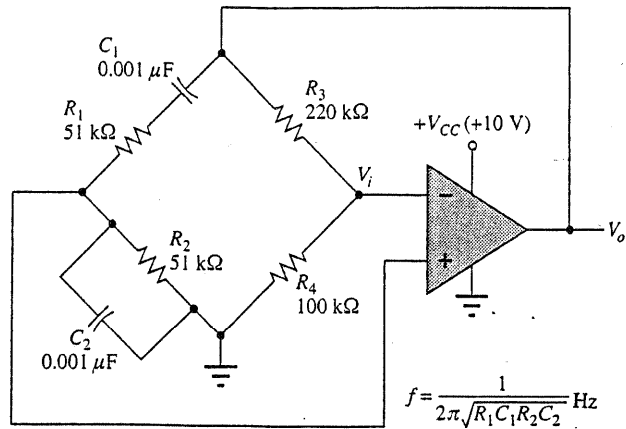


Figure 31-2

If $R_1 = R_2 = R$, and $C_1 = C_2 = C$, then

$$f = \frac{1}{2\pi RC} \text{ Hz} \tag{31.3}$$

Square-Wave Oscillator

A 555 Timer IC is a versatile linear digital IC which can be wired for operation as an oscillator, as shown in Fig. 31.3. The output resulting from this circuit is a pulse clock waveform of frequency

$$f = \frac{1.44}{(R_A + 2R_B)C} \text{ Hz} \tag{31.4}$$

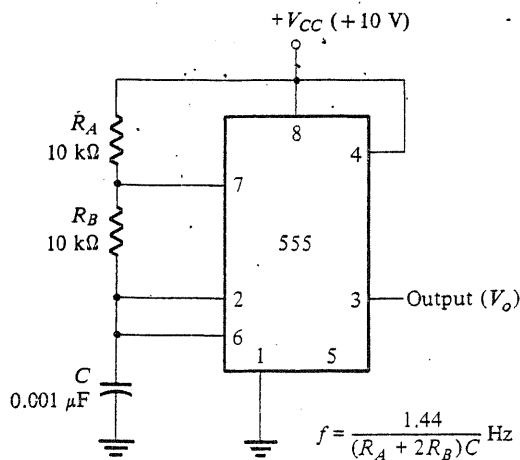


Figure 31-3

Schmitt-Trigger Oscillator

A single Schmitt-trigger IC, resistor, and capacitor can be used to build a pulse-type oscillator circuit, as shown in Fig. 31.4. The oscillator frequency is generally calculated using

$$f = \frac{k}{RC} \text{ Hz} \quad (31.5)$$

where k is typically 0.3 to 0.7, depending on the internal triggering levels of the Schmitt-trigger IC.

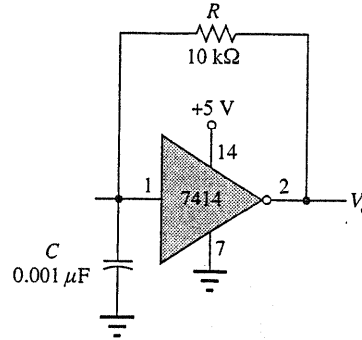


Figure 31-4

PROCEDURE

Part 1. Phase-Shift Oscillator

- Construct the circuit of Fig. 31.1 with a $R_F = 500 \text{ k}\Omega$ potentiometer, $R_1 = 22 \text{ k}\Omega$, $R = 100 \text{ k}\Omega$ and $C = 0.001 \text{ }\mu\text{F}$. (Measure and record the resistor values in Fig. 31.1.)
- Use the oscilloscope to record the output waveform of the oscillator circuit in Fig. 31.5. Adjust R_F for maximum undistorted output waveform, V_o . Record value of R_F for this undistorted condition.

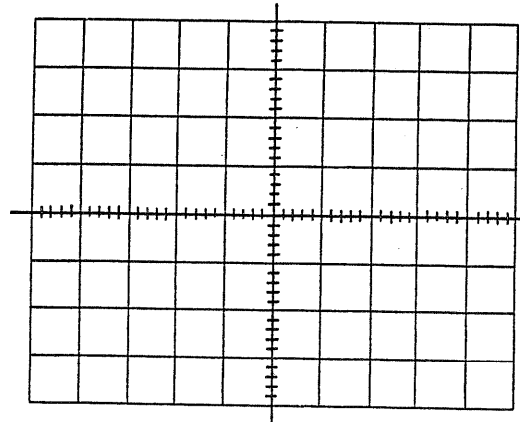


Figure 31-5

$$R_F \text{ (measured)} = \underline{\hspace{2cm}}$$

- c. Measure and record the time for one cycle of the waveform.

$$T \text{ (Period) (measured)} = \underline{\hspace{2cm}}$$

- d. Determine the frequency of the waveform.

$$f \text{ (Frequency)} = 1/T = \underline{\hspace{2cm}}$$

- e. Replace the capacitors with $C = 0.01 \mu\text{F}$ and repeat steps 1(c) through 1(d).

$$T \text{ (Period) (measured)} = \underline{\hspace{2cm}}$$

$$f \text{ (Frequency)} = 1/T = \underline{\hspace{2cm}}$$

- f. Calculate the theoretical frequency using Eq. 31.1 for both capacitor values.

$$f(C = 0.001 \mu\text{F}) \text{ (calculated)} = \underline{\hspace{2cm}}$$

$$f(C = 0.01 \mu\text{F}) \text{ (calculated)} = \underline{\hspace{2cm}}$$

Compare the measured and calculated frequencies for both capacitor values.

Part 2. Wien Bridge Oscillator

- a. Construct the circuit of Fig. 31.2. (Measure and record the resistor values in Fig. 31.2.)

- b. Using the oscilloscope observe and record the output waveform in Fig. 31.6.

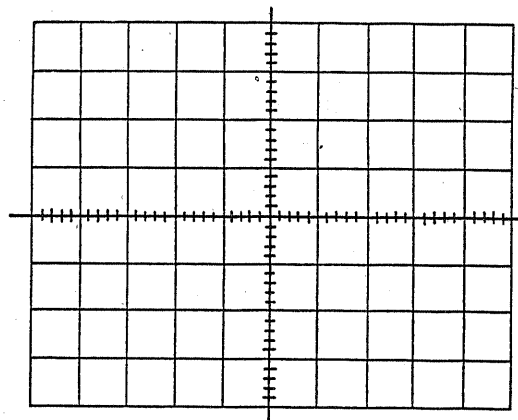


Figure 31-6

- c. Measure the time for one cycle.

T (measured) = _____

- d. Determine the signal frequency.

$f = 1/T =$ _____

- e. Change both capacitors to $C = 0.01 \mu\text{F}$ and repeat steps 2(c) through 2(d).

T (measured) = _____
 $f = 1/T =$ _____

- f. Calculate the theoretical frequency of the oscillator for each capacitor value.

$$f(C = 0.001 \mu\text{F}) \text{ (calculated)} = \underline{\hspace{2cm}}$$

$$f(C = 0.01 \mu\text{F}) \text{ (calculated)} = \underline{\hspace{2cm}}$$

Compare the calculated frequencies for both capacitor values with those measured.

Part 3. 555 Timer Oscillator

- Construct the oscillator circuit of Fig. 31.3. (Measure and record the resistor values in Fig. 31.3.)
- Observe and record the output waveforms at pins 3 and 4 in Fig. 31.7.

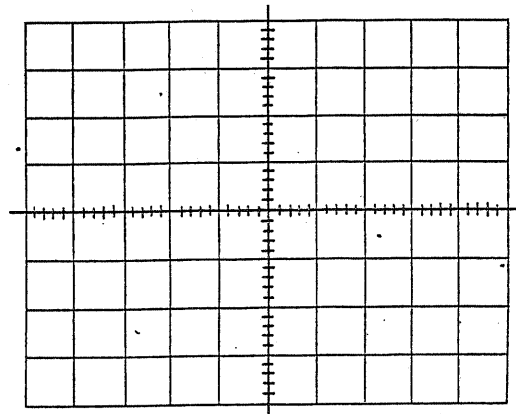


Figure 31-7

- Measure the period of the output waveform.

$$T \text{ (measured)} = \underline{\hspace{2cm}}$$

- d. Determine the signal frequency.

$$f = 1/T = \underline{\hspace{2cm}}$$

- e. Replace the capacitor with $C = 0.01 \mu\text{F}$, and repeat steps 3(c) through 3(d).

$$T \text{ (measured)} = \underline{\hspace{2cm}}$$

$$f = 1/T = \underline{\hspace{2cm}}$$

- f. Calculate the value of coefficient k using the measured values of f , R and C .

$$k \text{ (measured)} = \underline{\hspace{2cm}}$$

Use the value of k to calculate the theoretical value of frequency with the $C = 0.01 \mu\text{F}$ capacitor.

$$f \text{ (calculated)} = \underline{\hspace{2cm}}$$

Compare the calculated value of f for $C = 0.01 \mu\text{F}$ with that measured.

Part 4. Schmitt-Trigger Oscillator

- a. Construct the oscillator circuit of Fig. 31.4. (Measure and record the resistor value in Fig. 31.4.)

- b. Observe and record the output waveforms at pins 1 and 2 in Fig. 31.8.

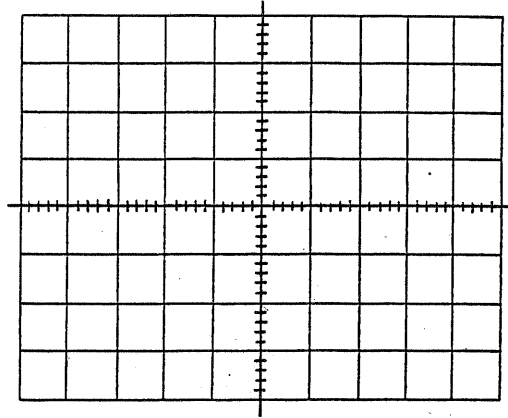


Figure 31-8

- c. Measure the period of the output waveform.

$$T \text{ (measured)} = \underline{\hspace{2cm}}$$

- d. Determine the signal frequency.

$$f = 1/T = \underline{\hspace{2cm}}$$

- e. Replace the capacitor with $C = 0.01 \mu\text{F}$, and repeat steps 4(c) through 4(d).

$$T \text{ (measured)} = \underline{\hspace{2cm}}$$

$$f = 1/T = \underline{\hspace{2cm}}$$

- f. Calculate the theoretical frequency, f , using Eq. 31.5 for each of the capacitor values.

$$f(C = 0.001 \mu\text{F}) \text{ (calculated)} = \underline{\hspace{2cm}}$$

$$f(C = 0.01 \mu\text{F}) \text{ (calculated)} = \underline{\hspace{2cm}}$$

Compare the calculated value of f for each capacitor with those measured.